

Que. No. 5

- a) The Boolean expressions simplifies to: (6 M)
- $(A + B) \cdot (A' + B)'$
 - $(X + Y) \cdot (X + Y')$
 - $(B + BC) (B + B'C) (B + D)$
- b) Find the simplest equation which implements the K-map represented by the following Sum of Products expression of logic function $f(W, X, Y, Z) = \Sigma (0, 1, 2, 8, 11) + d (3, 9, 15)$. (4 M)
- c) Find the simplest equation which implements the K-map shown below is (2 M)

	$\bar{C}$	C
$\bar{A} \bar{B}$	0	0
$\bar{A} B$	1	1
$A \bar{B}$	1	1
$A B$	0	1

Que. No. 6

- a) Implement the Boolean functions: (6 M)
- $F = x'y'z + x'yz' + xyz' + xyz$ using a 4:1 MUX
 - $F = A'B'C'D + A'B'CD + A'BC'D' + AB'CD + ABC'D' + ABCD' + ABCD$ using an 8:1 MUX
- b) Design four bit Binary to Gray Code Converter. (6 M)

***** All the Best *****

**DR. BABASAHEB AMBEDKAR TECHNOLOGICAL UNIVERSITY, LONERE –
RAIGAD -402 103
Semester Examination – December - 2019**

Branch: Electrical and Electronics Engineering
Subject:- Analog and Digital Electronics (BTEEE406B)
Date:- 04/12/2019

Sem.:- IV
Marks: 60
Time:- 3 Hr.

Instructions to the Students


- Each question carries 12 marks.
- Attempt **any five** questions of the following.
- Illustrate your answers with neat sketches, diagram etc., wherever necessary.
- If some part or parameter is noticed to be missing, you may appropriately assume it and should mention it clearly

Que. No. 1

- a) How transistor is used as an amplifier. (4 M)
- b) Explain Crossover Distortion in Amplifiers. (8 M)

Que. No. 2

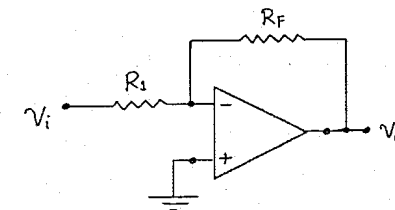- a) List and State any four characteristics of an ideal OPAMP. (4 M)
- b) Explain inverting amplifier configuration of an operational amplifier and derive the expressions for its gain. (4 M)
- Find the gain of the inverting amplifier shown below, Consider $R_1 = 1k\Omega$ and $R_F = 10k\Omega$.




For the circuit shown, if the OP-AMP can source maximum of 15mA current, then find the maximum current that the circuit can deliver to next stage. when

- $R_F:R_1 = 1k\Omega:100\Omega$.
- $R_F:R_1 = 10k\Omega:1k\Omega$.
- $R_F:R_1 = 100k\Omega:10k\Omega$

Assume maximum swing of OP-AMP = 0 to 10 V.

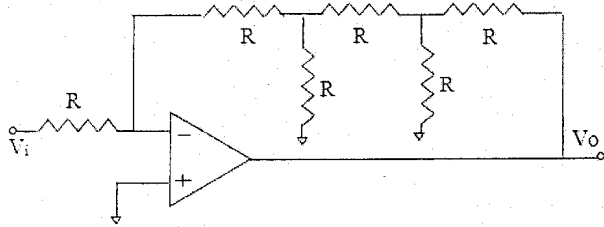- c) Find the gain of the circuit shown below, (4 M)




Que. No. 3

- a) Convert the given numbers into equivalent numbers of their other number systems. (4 M)


Decimal	Binary	Octal	Hexa-decimal
33			
	1110101		
		703	
			1AF

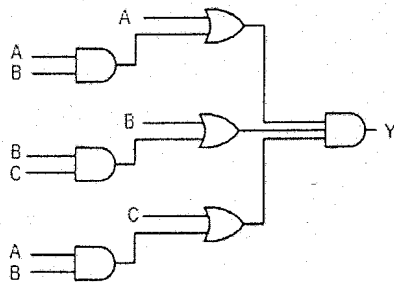- b) How many minimum numbers of 2-input NAND gates are required for implementing a 2-input XOR and XNOR functions and also draw their equivalent logic gates diagram using NAND gates only. (4 M)
- i) State the De-Morgan's theorem of Boolean algebra and Simplify complement of the function $X + YZ$ using De-Morgan's theorem. (4 M)
- ii) Which gate is equivalent to the given circuit?




Que. No. 4

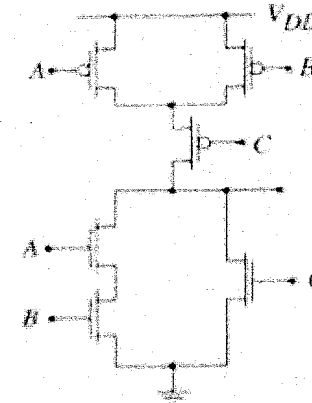- a) Convert the flipflops: (6 M)
- SR to D
 - JK to T
- b) Which logic function is implemented by CMOS complex logic structure shown in figure below? (4 M)
-



ii)

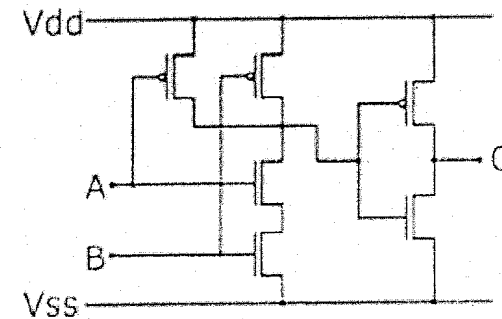

- c) The Boolean expression $f(A,B,C,D) = \Sigma (3, 7, 11, 13, 14, 15)$ simplifies to: (2 M)