DR. BABASAHEB AMBEDKAR TECHNOLOGICAL UNIVERSITY,

LONERE - RAIGAD - 402 103

Summer Semester Examination, May 2018

Branch: M. Tech. (Electrical Power Systems / Electrical Engineering) Semester: II Subject with Subject Code: ADVANCE POWER SYSTEM PROTECTION Marks: 60 [MTEE202/MTEPS202] Date: 16 / 05/ 2018 Time: 3 Hrs. Instructions to the Students: 1. Each question carries 12 marks. 2. Attempt any five questions of the following. 3. Illustrate your answers with neat sketches, diagram etc., wherever necessary. 4. If some part/parameter noticed to be missing, you may appropriately assume it and should mention it clearly. 5. Right side figure indicates the Marks carried by the questions. Draw and explain the basic construction of static relay along with advantages. [12] Q.1[12] Q.2Solve the following questions. (Any One) Explain the terms Transfer or Replica Impedance and Mixing transformers of circuits related (a) with the static relays in details. Prove the duality between the phase and amplitude comparator for Two input signals. (b) [12] Q.3Attempt the following questions. (Any Two) What are the different types of phase comparator and explain the direct or block-spike phase (a) comparator. Explain in detail the Hall effect device as a vector product phase comparator. Draw the block diagram and explain the instantaneous measuring relays for voltage and current and give the application of the over and under voltage relays. Solve the following questions. Q.4 [06] What do you understand by duo-bias Transformer differential protection? Explain it in detail. (a) [06] Explain the harmonic restraint percentage differential relays for transformer protection. (b) Answer the following questions. Q.5Draw a schematic diagram, operating characteristic and explain the working of a static mho [06] (a) relay using an amplitude comparator. [06] Explain the effects of power swings on the performance of the distance relay. Answer the following questions. Q.6 Discuss the on line digital computer application for the protection of the transmission line. [06] (a) Draw and explain the micro-processors based overcurrent relay for phase and earth faults. [06] (b)

-----%%%@@@@@%%%-----