

DR. BABASAHEB AMBEDKAR TECHNOLOGICAL UNIVERSITY, LONERE
End Semester Examination – Winter 2018

Course: B. Tech in Electrical Engineering
 Subject Name: Network Analysis and Synthesis
 Date: 03/12/2018

Max Marks: 60

Semester: III
 Subject Code: BTEEC302
 Duration: 3 Hrs

Instructions to the Students:


1. Solve ANY FIVE questions out of the following
2. Students should note, no supplement will be provided.
3. Use of non-programmable scientific calculators is allowed.
4. Assume suitable data wherever necessary and mention it clearly.

Marks

Q.1 Solve Any Two sub questions

A) Use superposition theorem to find current through branch A-B in the Circuit of figure

06

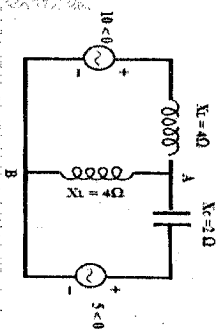

B) Explain the following terms
 i) Independent and Dependent sources
 ii) Lumped and distributed systems

06


C) State and Explain maximum Power transfer theorem in case A.C circuits

06

Q.2 Solve Any Two sub questions

A) Using Nodal Analysis find Voltage ' V_x ' for given N/W

06

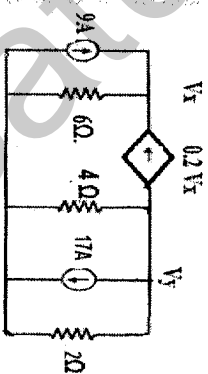


06

B) Explain Concept of Complex Frequency in detail

06

Q. 5 Solve All Sub-Questions

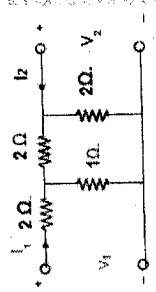A) Determine the Open circuit parameters for the circuit shown below



06

B) What is the physical significance of Pole and Zero in a transfer function?

06

Q. 6 Solve All Sub-Questions

A) What is Meant by Resonance in RLC Series Circuit and Derive equation for resonant Frequency

04

B) Explain the High pass filter and band pass filter.


02

C) A Coil of inductance 31.8mH and resistance of 10Ω is connected in parallel across $250\text{V}, 50\text{Hz}$. Determine value of Capacitance so that total current is in phase supply voltage

*** End ***

06

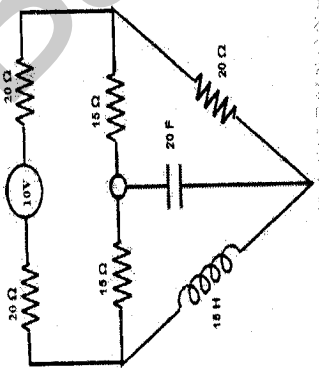B) Obtain dual network for the circuit given below



06

C) Define the following

- i. Planner graph
- ii. NonPlanner graph
- iii. Subgraph.
- iv. Tree and Co-Tree


06

Q. 3 Solve All Sub-Questions

A) Explain response of RL series circuit to D.C. excitation

06

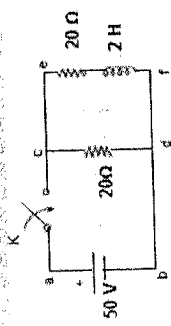B) Find the expression of current when 50V dc source is applied as switch K is opened At $t=0$.



06

Q. 4 Solve All Sub-Questions

A) Find the Laplace transform of the waveform

